

TELEPHONE RING DETECTOR WITH RELAY OUTPUT



K8086

Simply connect in parallel with phone line. Accepts standard adaptor & telephone plug.



Features:

- ☑ simply connect in parallel with phone line
- ☑ powerful led flashes when phone rings
- ☑ the unit will feature a relay output if connected to a 12VDC power supply
- ☑ relay output: continuous or on/off to the rhythm of ringing of the telephone
- great for noisy environments, for the hearing impaired, as addional ringer, to replace existing ringer, ...
- ☑ accepts standard adaptor & telephone plug

Specifications:

- 10.000 mcd led!
- connects to PSTN line
- RJ11 connector
- supply: 12VDC/100mA adapter (Ex. <u>PS1203</u>)
- output Contact (NO): 1A max.
- dimensions: 80x55x35mm / 3,15 x 2,16 x 1,37"

Includes:

- · attractive enclosure
- · adhesive strips for easy fixing



1. Assembly (Skipping this can lead to troubles!)

Ok, so we have your attention. These hints will help you to make this project successful. Read them carefully.

1.1 Make sure you have the right tools:

- . A good quality soldering iron (25-40W) with a small tip.
- Wipe it often on a wet sponge or cloth, to keep it clean; then apply solder to the tip, to give it a wet look. This is called 'thinning' and will protect the tip
 and enables you to make good connections. When solder rolls off the tip, it needs cleaning.
- Thin raisin-core solder. Do not use any flux or grease.
- A diagonal cutter to trim excess wires. To avoid injury when cutting excess leads, hold the lead so they cannot fly towards the eyes.
- Needle nose pliers, for bending leads, or to hold components in place.
- Small blade and Phillips screwdrivers. A basic range is fine.



For some projects, a basic multi-meter is required, or might be handy


· O

1.2 Assembly Hints :

- ⇒ Make sure the skill level matches your experience, to avoid disappointments.
- ⇒ Follow the instructions carefully. Read and understand the entire step before you perform each operation.
- ⇒ Perform the assembly in the correct order as stated in this manual
- ⇒ Position all parts on the PCB (Printed Circuit Board) as shown on the drawings.
- ⇒ Values on the circuit diagram are subject to changes, the values in this assembly guide are correct*
- ⇒ Use the check-boxes to mark your progress.
- ⇒ Please read the included information on safety and customer service
- * Typographical inaccuracies excluded. Always look for possible last minute manual updates, indicated as 'NOTE' on a separate leaflet.

1.3 Soldering Hints:



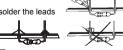


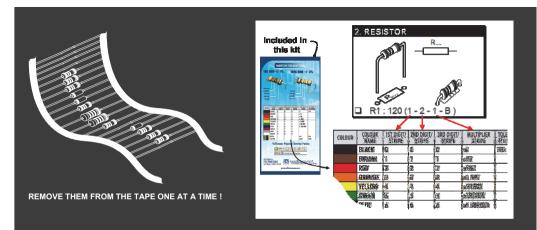- 2- Make sure the solder joints are cone-shaped and shiny
- 3- Trim excess leads as close as possible to the solder joint









DO NOT BLINDLY FOLLOW THE ORDER OF THE COMPONENTS ONTO THE TAPE.

ALWAYS CHECK THEIR VALUE ON THE PARTS LIST!



3. Resistors

1. Diodes. Watch the polarity!



4. IC socket, Watch the position of the notch!



7. Transistor



2. Zener diodes. Watch the polarity!




5. Vertical diodes. Watch the polarity!



6. Pinheader + shunt




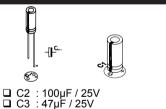
8. Electrolytic Capacitors. Watch the polarity!





- 100K

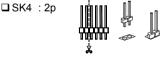

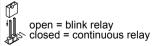

9. Terminal blocks











11. LED. Watch the polarity!

LD1 : 5mm (super red)

*/- 13mm

*/- 11mm

Anode Cathode

12. Modular Jack




15. IC, watch the position of the notch!

☐ IC1 :4N27



13. Capacitor

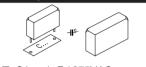


□ C1 : 1µF / 275VAC

14. Relay






16. Connection examples

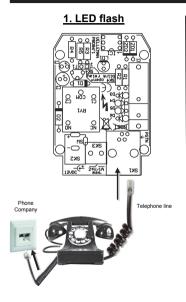


2. LED flash + relay ouput

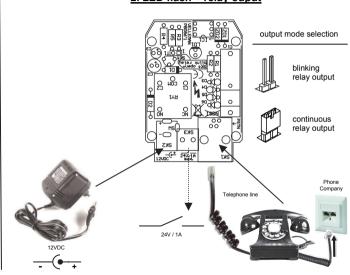




17. Assembly

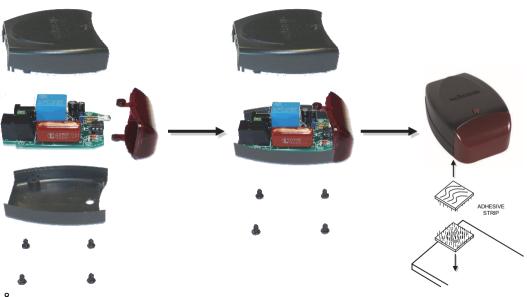




Schematic diagram.

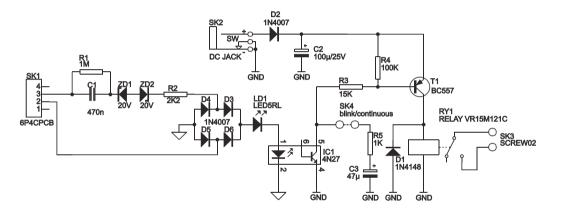

PCB

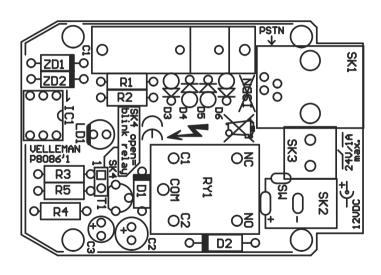

VELLEMAN NV Legen Heirweg 33 9890 Gavere Belgium Europe www.velleman.be www.velleman-kit.com





VELLEMAN NV Legen Heirweg 33, B-9890 GAVERE Belgium (Europe)

梦 @ velleman_RnD

